

Solution

- The dc term is

$$I_0 = \frac{V_0}{R} = \frac{10}{5} = 2 \text{ A}$$


- AC current terms are computed from phasor analysis:

$$I_1 = \frac{V_1}{R + j\omega_1 L} = \frac{20 \angle (-25^\circ)}{5 + j(2\pi 60)(0.015)} = 2.65 \angle (-73.5^\circ) \text{ A}$$

$$I_2 = \frac{V_2}{R + j\omega_2 L} = \frac{30 \angle 20^\circ}{5 + j(4\pi 60)(0.015)} = 2.43 \angle (-46.2^\circ) \text{ A}$$

- Load current then can be calculated as

$$i(t) = 2 + 2.65 \cos(2\pi 60t - 73.5^\circ) + 2.43 \cos(4\pi 60t - 46.2^\circ) \text{ A}$$

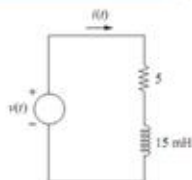


Exercise 12

- A non-sinusoidal voltage source has a fourier series of

$$v(t) = 10 + 20 \cos(2\pi 60t - 25^\circ) + 30 \cos(4\pi 60t + 20^\circ) \text{ V}$$

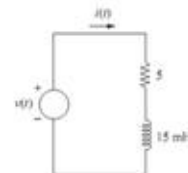- This voltage is connected to a load that is 5 ohm resistor and 15 mH inductor in series.
- Determine the power absorbed by the load.



Solution (cont.)

- The power at each frequency in the Fourier series can be determined as follows.

dc term: $P_0 = (10 \text{ V})(2 \text{ A}) = 20 \text{ W}$

$$\omega = 2\pi 60: P_1 = \frac{(20)(2.65)}{2} \cos(-25^\circ + 73.5^\circ) = 17.4 \text{ W}$$

$$\omega = 4\pi 60: P_2 = \frac{(30)(2.43)}{2} \cos(20^\circ + 46^\circ) = 14.8 \text{ W}$$

- Total power is then

$$P = 20 + 17.4 + 14.8 = 52.2 \text{ W}$$

- Alternative Method:** Since the average power of inductor is zero, the power absorbed by the load can be calculated using rms current as follows

$$P = I_{\text{rms}}^2 R = \left[2^2 + \left(\frac{2.65}{\sqrt{2}} \right)^2 + \left(\frac{2.43}{\sqrt{2}} \right)^2 \right] 5 = 52.2 \text{ W}$$

